

Novel Waveform Generation Using HL9404 Broadband Balun, HL9462 Z-Matched Pick-Off Tee, and HL9474 6dB Resistive Power Divider

Madrone Coopwood, Jason Yoho, Ph.D.

OVERVIEW

This application note demonstrates use of HYPERLABS' broadband coaxial components as general-purpose analog signal processing components for the generation of novel time-domain waveforms. The HL9474 6dB resistive power divider and HL9462 Z-matched pick-off tee are demonstrated as lossy broadband summing networks and the HL9404 broadband balun is demonstrated as a pulse inverter and 180° signal splitter. The HL5567 PAM4 Encoder is used to combine two PRBS patterns into PAM4 signaling. Utilizing the basic arithmetic functions of addition, inversion, and subtraction, together with a time delay, a wide variety of novel broadband waveforms are generated.

This application note builds on prior work reported in Picosecond Pulse Labs (PSPL) Application Note AN-20a_[1]. In the referenced note, Jim Andrews, Ph.D. used PSPL pulse generators together with PSPL passive components to produce a variety of novel waveforms. A similar set of waveforms are demonstrated at higher bandwidths in this application note utilizing HYPERLABS' industry leading broadband passive components.

APPLICATIONS

The waveforms demonstrated in this application note are useful for a variety of applications ranging from UWB Imaging to Data Communications.

UWB MONOCYCLE

Starting with a 20 ps full width half max (FWHM) single-ended positive impulse, a UWB monocycle is generated. First, HL9404 Broadband Balun is used to create a differential impulse. Next, the negative impulse is delayed by 20 ps and added to the positive impulse using a HL9474 Resistive Power Divider, as shown in *Figure 1*. *Figures 2 – 5* show the actual measurements of the various pulses made by the block diagram shown in *Figure 1*.

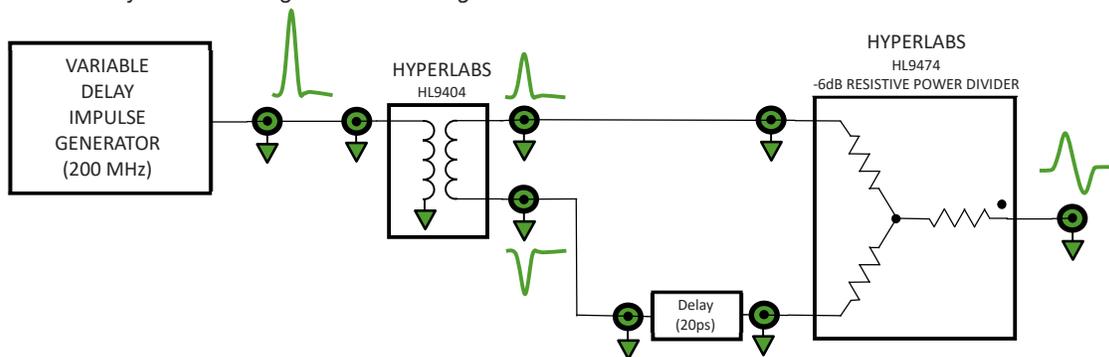


Figure 1. Block Diagram of UWB Monocycle Generator

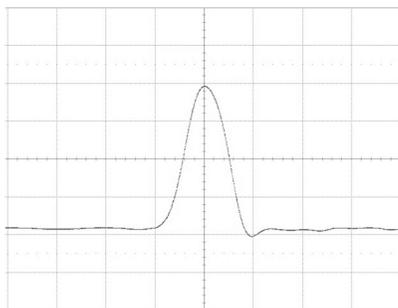


Figure 2. Input Impulse at 100mV/div & 20ps/div

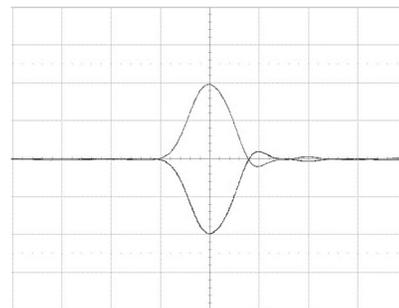


Figure 3. HL9404 Outputs at 100mV/div & 20ps/div

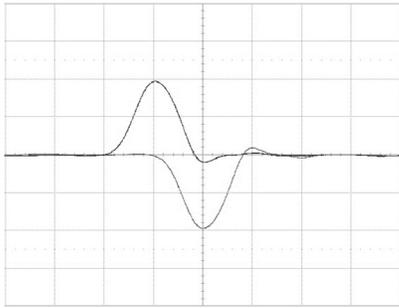


Figure 4. Negative Balun Output Delayed by 20ps

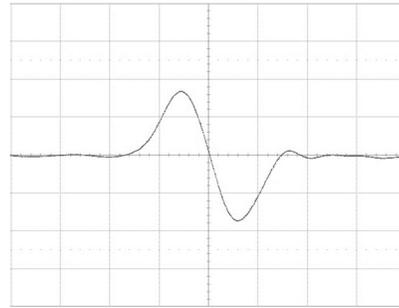


Figure 5. Summed Output at 50mV/div & 20ps/div

PRE-DISTORTED PULSES

Using a resistive power divider, a narrow impulse can be added or subtracted from a rectangular pulse to create various waveform defects such as precursor, overshoot, and trailing edge undershoot. The techniques demonstrated below can be used to pre-distort waveforms and compensate for distortion products generated elsewhere in the system.

Once again, the HL9404 Broadband Balun was used to create a differential impulse. The HL9462 Z-Matched Pick-Off Tee was used as a weighted (unequal) summing network as shown in Figure 6 below.

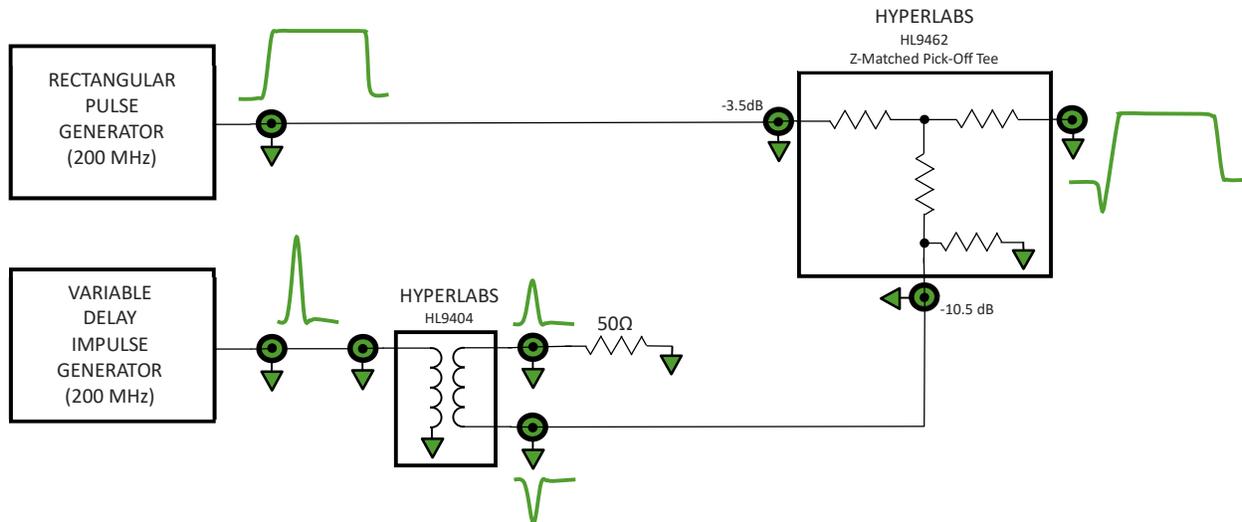


Figure 6. Block Diagram of Pre-Distorted Pulse Generator.

A 20 ps wide negative impulse was summed with a 200 ps wide rectangular pulse to create the first series of pre-distorted pulse waveforms. Each pulse source was set to 400 mVp-p amplitude and 200 MHz repetition rate. The input pulses are shown in Figure 7 and Figure 8. The relative delay between the impulse and rectangular pulse generators was adjusted to position the effect of the impulse at various locations on the rectangle pulse.

The single-ended insertion loss of HL9404 Broadband Balun is typically 6 dB. The pick-off port of HL9462 typically has 10.5 dB loss compared to 3.5 dB loss at the thru port, a difference of 7 dB. The impulse is thus attenuated by ~13 dB relative to the rectangular pulse (6 dB in the balun and 7 dB in the pick-off tee) resulting in ~20% precursor as shown in Figure 9. By increasing the relative delay of the impulse generator, the negative impulse can be re-positioned to give an interference drop-out in the middle of the rectangle pulse as shown in Figure 10 or a trailing edge undershoot as shown in Figure 11.

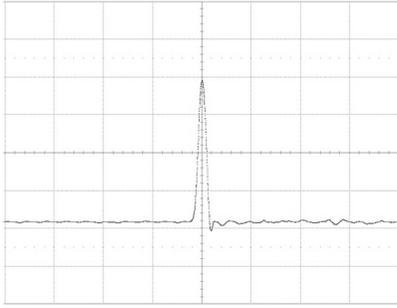


Figure 7. Input Impulse. 100mV/div & 100ps/div

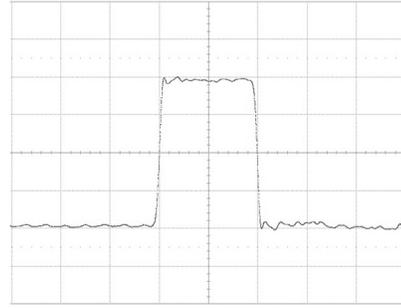


Figure 8. Input Rectangle Pulse. 100mV/div & 100ps/div

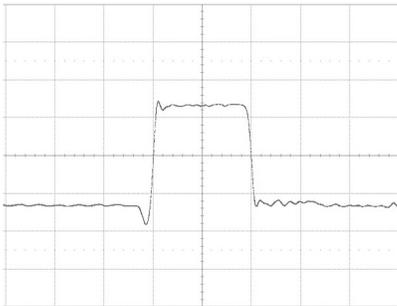


Figure 9. Rectangular Pulse with 20% precursor.
100mV/div & 100ps/div

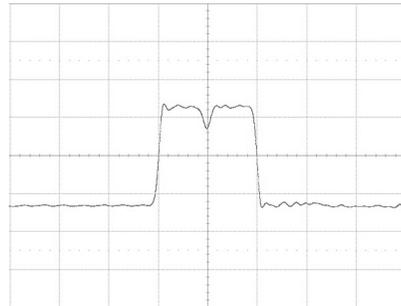


Figure 10. Rectangular Pulse with interference drop-out.
100mV/div & 100ps/div

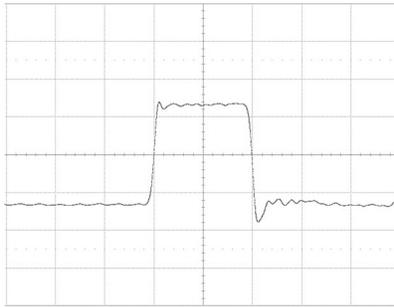


Figure 11. Rectangular Pulse with 20% trailing edge undershoot. 100mV/div & 100ps/div

To generate positive going aberrations on the rectangle pulse as shown in *Figure 12* and *Figure 13*, the generator is simply re-configured connecting the positive output of the balun to the pick-off port as shown in *Figure 14*.

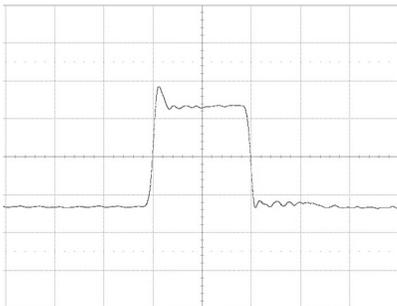


Figure 12. Rectangular Pulse with 20% overshoot.
100mV/div & 100ps/div

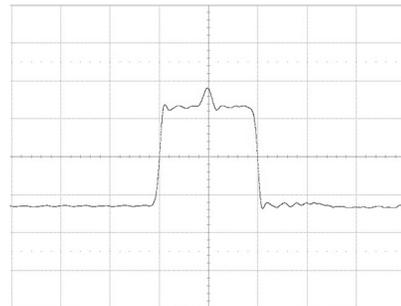


Figure 13. Rectangular Pulse with 20% interference spike.
100mV/div & 100ps/div

By adjusting the impulse delay, the impulse can be positioned to generate an overshoot as in *Figure 12* or an interference spike as shown in *Figure 13*.

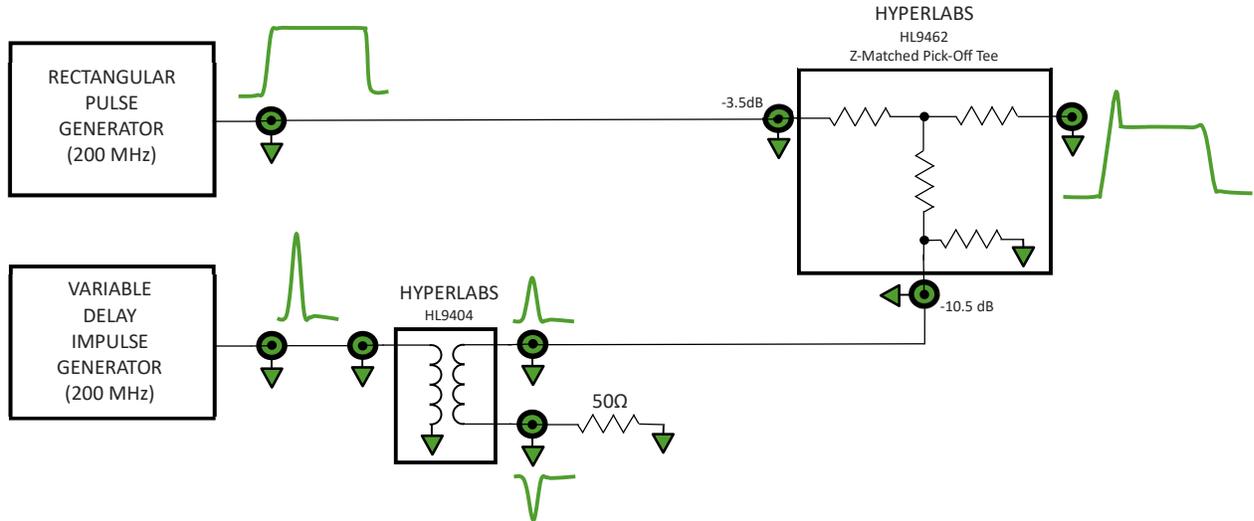


Figure 14. Block Diagram of Pre-Distorted Pulse Generator.

NOISE-LIKE PULSES (NLP)

A noise like pulse (NLP) is generated by summing a relatively high amplitude and narrow impulse on top of a rectangular pedestal or lower bandwidth Gaussian pulse. For this demonstration, an HL9474 6 dB power divider is used to sum the two input signals. A 6 dB attenuator is inserted in the path of the pedestal pulse to give the impulse 2x weighting over the pedestal.

Later in this application note, similar 2x weighted summation functionality is demonstrated using the HL9462 Z-Matched Pick-Off Tee without need for an external attenuator. A block diagram of the NLP Generator system is shown in *Figure 15*.

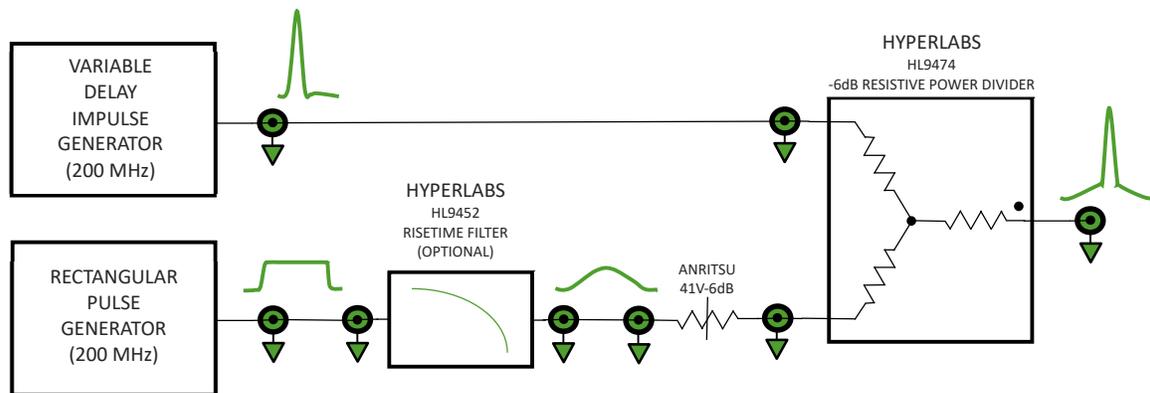


Figure 15. Block Diagram of Noise Like Pulse (NLP) Generator

The input signals are a 20 ps FWHM impulse and a 500 ps wide rectangular pulse, both running at 200 MHz repetition rate. Both inputs are shown in *Figure 16*.

First, the signals shown in *Figure 16* were added without a lowpass filter in the system, resulting in a rectangular pedestal NLP as shown in *Figure 17*.

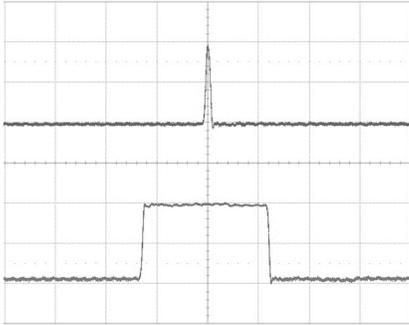


Figure 16. Input Signals for Noise Like Pulse Generator.
200mV/div & 200ps/div

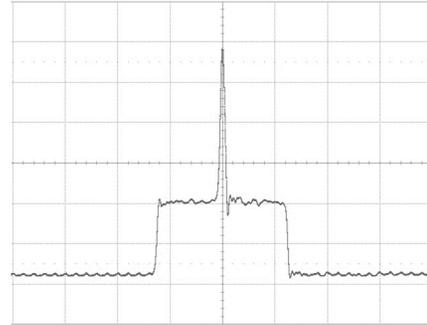


Figure 17. Noise Like Pulse with Rectangular Pedestal.
50mV/div & 200ps/div

Next, an HL9452-200 Risettime Filter was inserted in the path of the pedestal pulse. The HL9452-200 is a transition time converter. It converts the fast risetimes and falltimes of the rectangular pulse source into 200 ps transitions (10%-90%). The result is shown in Figure 18.

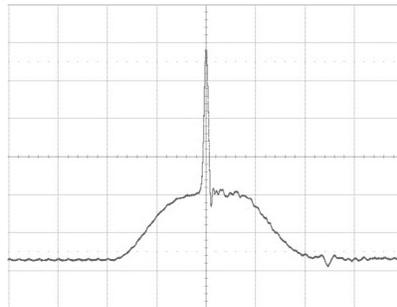


Figure 18. Noise Like Pulse with Pseudo-Gaussian Pedestal Pulse. 50mV/div & 200ps/div

100Gb/s PAM4 ENCODING

Two binary serial data streams can be summed to generate 4-level Pulse Amplitude Modulation (PAM4). In this broadband modulation scheme, the amplitude of the MSB is 2x the amplitude of the LSB. HYPERLABS' HL5567 PAM4 Encoders are a single component solution, perfectly suited to perform PAM4 encoding. Using two nearly equal amplitude NRZ serial data streams, the LSB is connected to the pick-off port and the MSB is connected to the input as shown in Figure 19.

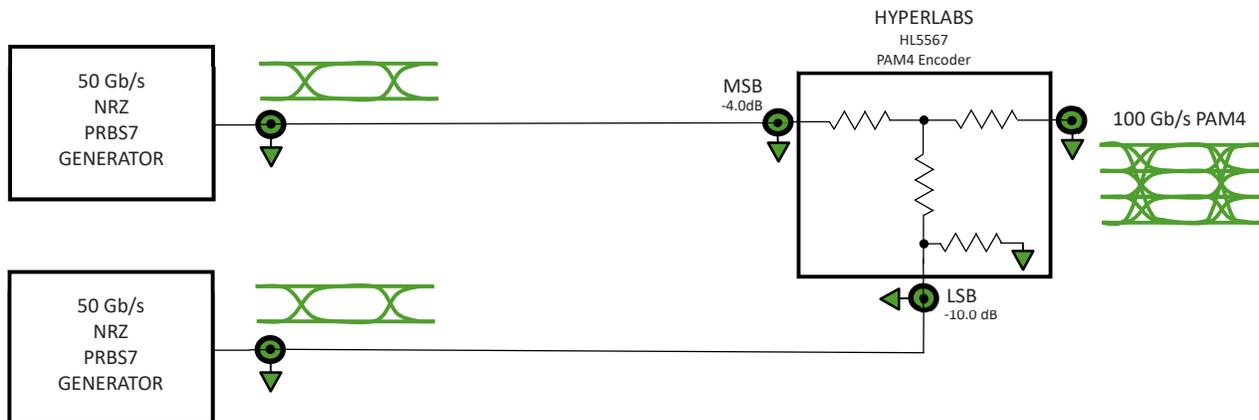


Figure 19. Block Diagram of PAM4 Encoder Test

As shown in *Figure 20*, two 50 Gb/s serial data streams were combined using an HL5567 PAM4 Encoder to create a 100 Gb/s PAM4 signal. The LSB and MSB data patterns were 7th order Pseudo-Random Binary Sequences (PRBS7). A PRBS7 data pattern is 127 bits long. The LSB data pattern was delayed by 39 bits relative to the MSB data pattern. The entire pattern length of each input signal is shown in *Figure 20*. Eye diagrams of the input signals are shown in figures 21 and 22.



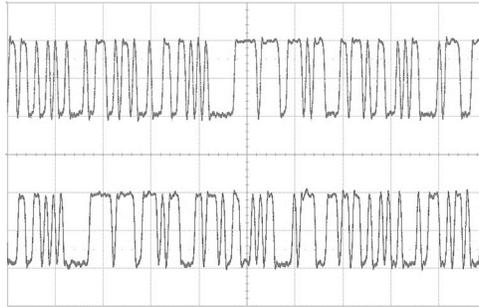


Figure 20. Input Data Patterns, 50 Gb/s, PRBS7, LSB(Top), MSB(Bottom). 200mV/div & 255ps/div

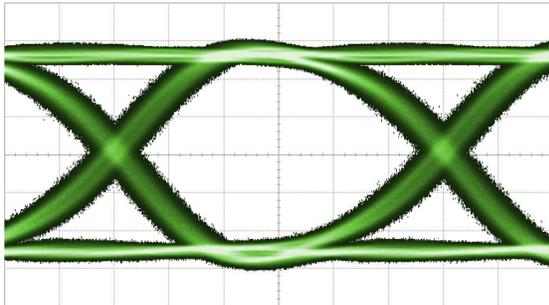

*Figure 21. LSB Input Eye Diagram, 50 Gb/s, PRBS7.
75mV/div & 3.35ps/div*

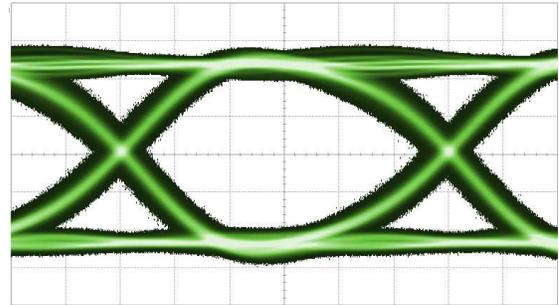

*Figure 22. MSB Input Eye Diagram, 50 Gb/s, PRBS7.
75mV/div & 3.35ps/div*

Output signals representing each input individually and in combination were examined. First, each input signal was connected to the HL5567 individually with the opposite input terminated into 50Ω. The corresponding binary output waveforms were captured and shown in *Figure 23 (Top and Middle)*. Finally, both input signals were connected simultaneously, and the combined PAM4 output waveform was captured and shown in *Figure 23 (Bottom)*. Output eye diagrams are presented in *Figures 24 - 26*.

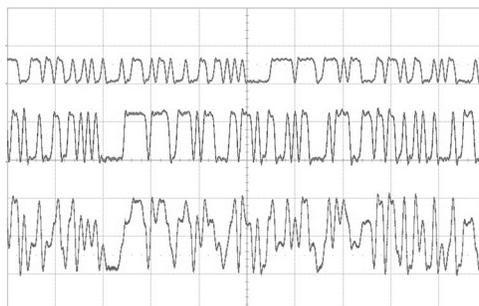


Figure 23. Output Data Patterns, LSB(Top), MSB(Middle), LSB+MSB(Bottom). 200mV/div & 255ps/div

As shown in *Figure 26*, the HL5567 PAM4 Encoder produces high quality 100 Gb/s PAM4 waveforms when driven from two high-quality 50 Gb/s PRBS7 binary patterns. Minor pattern dependencies were observed when tested at different bit shift values. Results will vary when used with real world data.

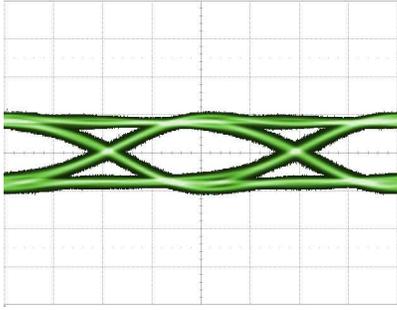


Figure 24. 50 Gb/s Output Eye Diagram. LSB port driven, MSB port terminated into 50Ω. 71mV/div & 5ps/div

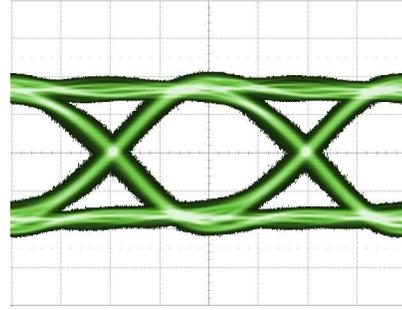


Figure 25. 50 Gb/s Output Eye Diagram. MSB port driven, LSB port terminated into 50Ω. 71mV/div & 5ps/div

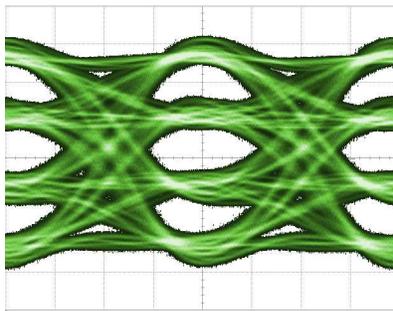


Figure 26. 100 Gb/s PAM4 Output Eye Diagram. LSB and MSB ports driven. 71mV/div & 5ps/div

It is important to keep in mind that the HL5567 PAM4 Encoder is a resistive passive network. This feature allows any data pre-emphasis to pass through the device without any non-linear effects.

CONCLUSION

HYPERLABS' broadband coaxial components provide arithmetic functionality at very high bandwidths. The HL9404, HL9462, HL9474, and HL5567 were demonstrated as general-purpose analog signal processing components for the generation of novel time-domain waveforms. Addition, inversion, subtraction, and weighted summation were demonstrated.

PHOTOS

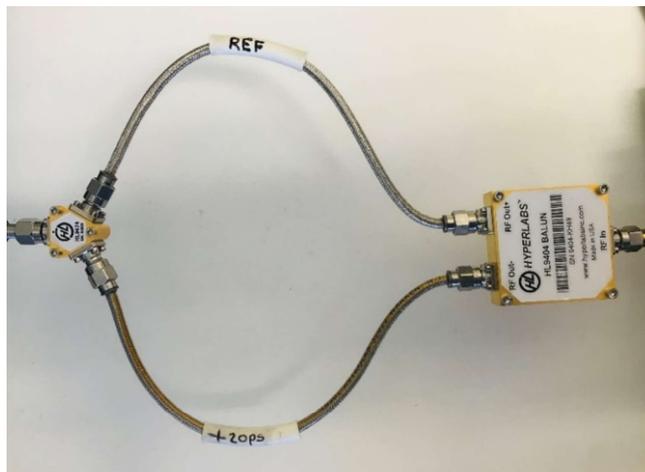


Figure 27. Photo of UWB Mono-Cycle Generator

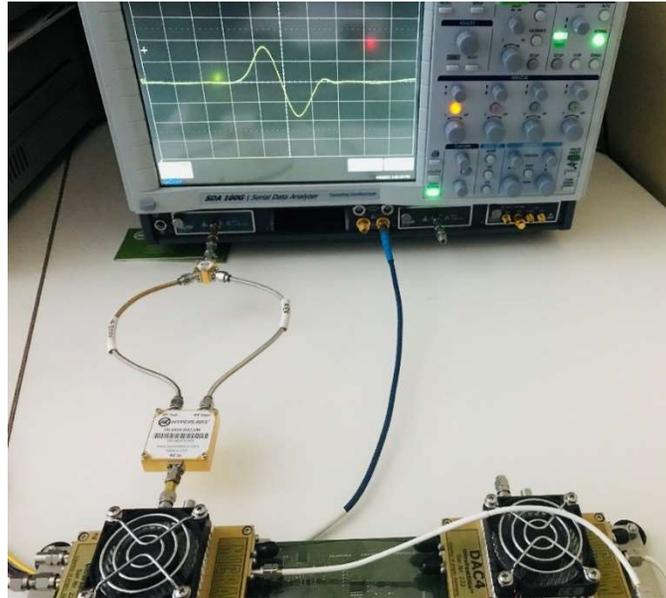


Figure 28. Photo of Monocycle Generator together with LeCroy SDA100G Sampling Oscilloscope, SE-50 Sampling Modules, and Dual-Channel Micram DAC4 Signal Source.



Figure 29. Photo of Pre-Distorted Pulse Generator